

Transfer Function


Outlines

- Basics of Transfer Function
- Types of Transfer Function
- Properties of Transfer Function
- Advantages of Transfer Function
- Disadvantages of Transfer Function

Engineering Funda

Basics of Transfer Function

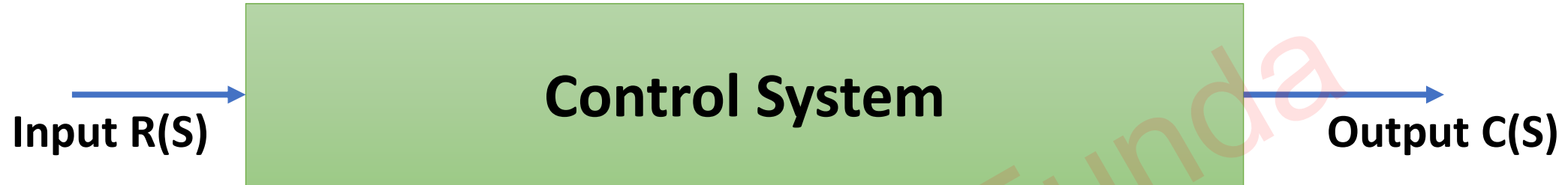
- Transfer Function gives the relationship between the input and the output of the system.



$$\Rightarrow T(s) = \frac{C(S)}{R(S)} = \frac{N(S)}{D(S)}$$

- Here, The Roots of N(S) gives details of Zeros of System and The Roots of D(S) gives details of Poles of System.
- Transfer Function usually represented in form of frequency domain {Laplace Transforms (Continuous Time Systems), Z Transforms (Discrete Time Systems)}.

Types of Transfer Function

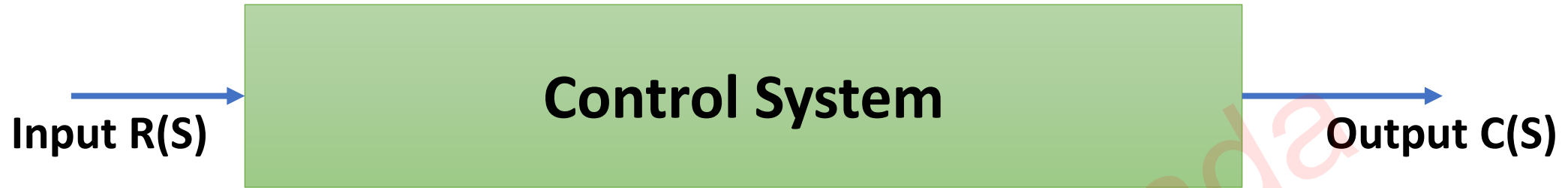

$$\Rightarrow T(s) = \frac{C(S)}{R(S)} = \frac{N(S)}{D(S)}$$

❑ Proper Transfer Function


- Poles $P >$ Zeros Z {Order of $D(S)$ is Greater then Order of $N(S)$.}

❑ Improper Transfer Function

- Poles $P <$ Zeros Z {Order of $D(S)$ is less then Order of $N(S)$.}

Properties of Transfer Function

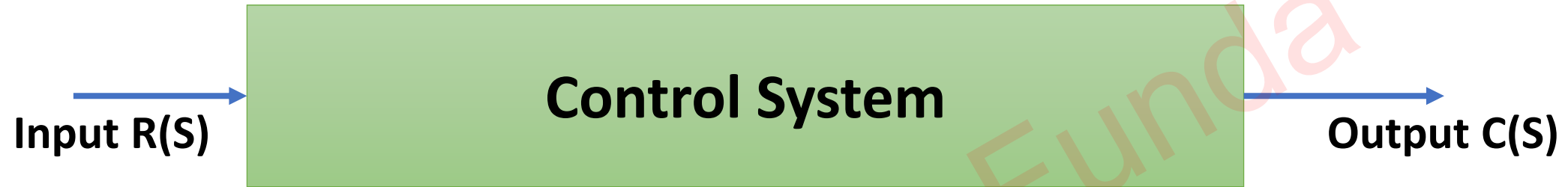- The Transfer Function of a system is the Laplace Transform of its Impulse Response for Zero Initial Conditions.



$$\Rightarrow T(s) = \frac{C(S)}{R(S)} = \frac{N(S)}{D(S)}$$

- The Transfer Function can be determined from Input – Output pair by taking ratio of Laplace Output to Laplace of Input.
- Practically, Transfer Function is Independent of the Inputs to the System.
- The Transfer Function can be defined only for LTI (Linear Time Invariant) System. For Non Linear System, response of the system changes with respect to time.
- Poles and Zeros of the System can be identified by Transfer Function.
- Characteristics and Stability of the System can be identified by Transfer Function.

Advantages of Transfer Function

- Transfer Function is a mathematical model that gives the gain of the given system.
- Integral and Differential Equations are converted to simple algebraic equation.
- From Transfer Function, Output of system can be identified for any Inputs.
- Transfer Function is dependent on system only, not on Inputs.
- Using Transfer Function, Poles, Zeros, Stability and Characteristics can be Identified.

Disadvantages of Transfer Function

- Transfer Function is only valid for LTI Systems.
- Transfer Function doesn't account for Initial Conditions.
- Transfer Function doesn't give any idea about how the present output is progressing.

Transfer Function From Differential Equation

Question 1 – If the Differential Equation is given by:

$$\Rightarrow \frac{d^2y}{dt^2} + \frac{dy}{dt} + y = 6x \quad \Rightarrow T(s) = \frac{Y(s)}{X(s)}$$

Where x is Input and y is Output.

Find, The Transfer Function of the given Differential Equation.

⇒ Apply Laplace x' form to differential eq.ⁿ

$$\Rightarrow [s^2 Y(s) - s y(0) - y'(0)] + [s Y(s) - y(0)] + Y(s) = 6 X(s)$$

⇒ Apply zero initial cond.ⁿ

$$\Rightarrow Y(s) [s^2 + s + 1] = 6 X(s)$$

$$\Rightarrow T(s) = \frac{Y(s)}{X(s)} = \frac{6}{s^2 + s + 1}$$

Question 2 – Find The Transfer Function of the given Differential Equation.

$$\Rightarrow Y'' = 5, Y(0) = 1, Y'(0) = 2$$

$$\Rightarrow X' = e^{-t}, X(0) = 0$$

Where Y is Output and X is Input.

⇒ Apply Laplace X' form to eqⁿ ①

$$\Rightarrow [s^2 y(s) - sy(0) - y'(0)] = 5/s$$

$$\Rightarrow [s^2 y(s) - s(1) - 2] = 5/s$$

$$\Rightarrow s^2 y(s) = \frac{5}{s} + s + 2$$

$$\Rightarrow s^2 y(s) = \frac{s^2 + 2s + 5}{s}$$

$$\Rightarrow y(s) = \frac{s^2 + 2s + 5}{s^3} \text{ — (A)}$$

⇒ Apply Laplace X' form to eqⁿ ②


$$\Rightarrow [sX(s) - X(0)] = \frac{1}{s+1}$$

$$\Rightarrow X(s) = \frac{1}{s(s+1)} \text{ — (B)}$$

$$\begin{aligned} \rightarrow T(s) &= \frac{y(s)}{X(s)} = \frac{s^2 + 2s + 5/s}{1/s(s+1)} \\ &= \frac{(s+1)(s^2 + 2s + 5)}{s^2} \end{aligned}$$

Transfer Function of RC Circuits

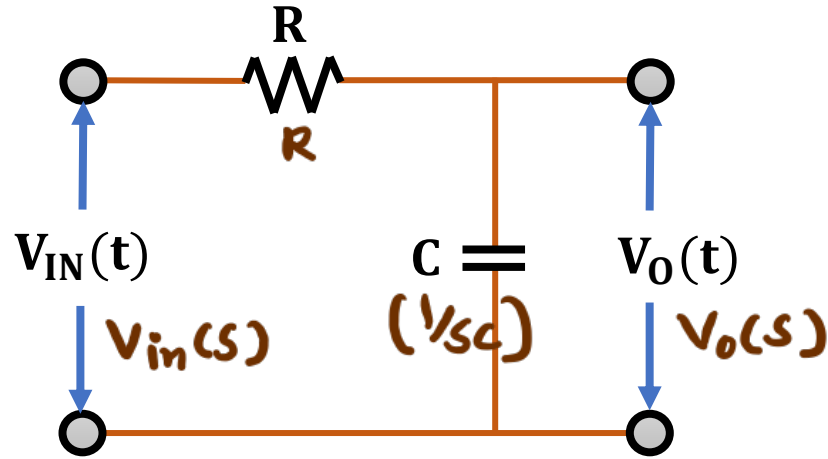Question 1 – Find the Transfer Function of a given (LPF) RC Circuit.



⇒ Zero initial cond.ⁿ


$$t=0, V_C = 0.$$

⇒ Transfer function $T(s) = \frac{V_o(s)}{V_{in}(s)}$

⇒ Apply voltage divider rule.


$$\Rightarrow V_o(s) = V_{in}(s) \left(\frac{1/sC}{R + 1/sC} \right)$$
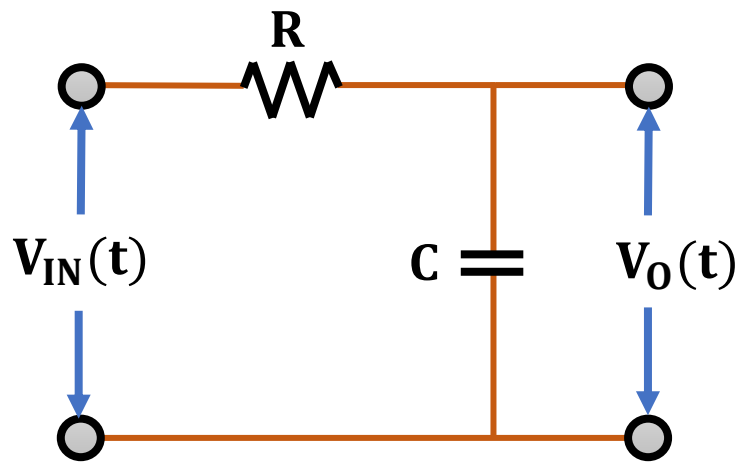
$$\Rightarrow \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{1}{1 + RSC}$$




$$\rightarrow X_C = 1/sC = \frac{1}{j\omega C}$$

$\rightarrow$ at $\omega \rightarrow \text{low}$, $X_C = \text{high (O.C.)}$, $V_p \rightarrow V_p$
at $\omega \rightarrow \text{high}$, $X_C = \text{low (S.C.)}$, $V_p \rightarrow 0$

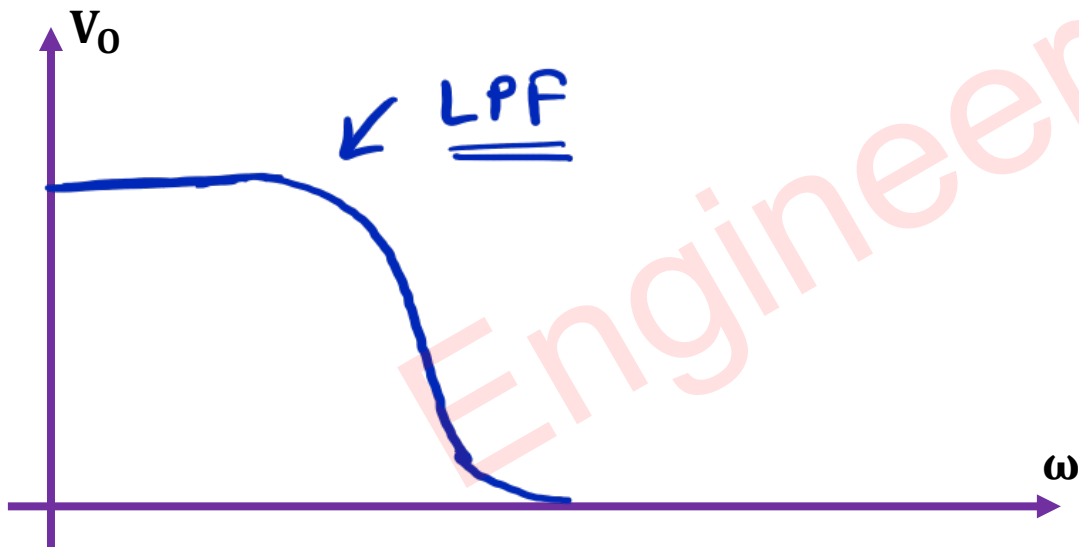

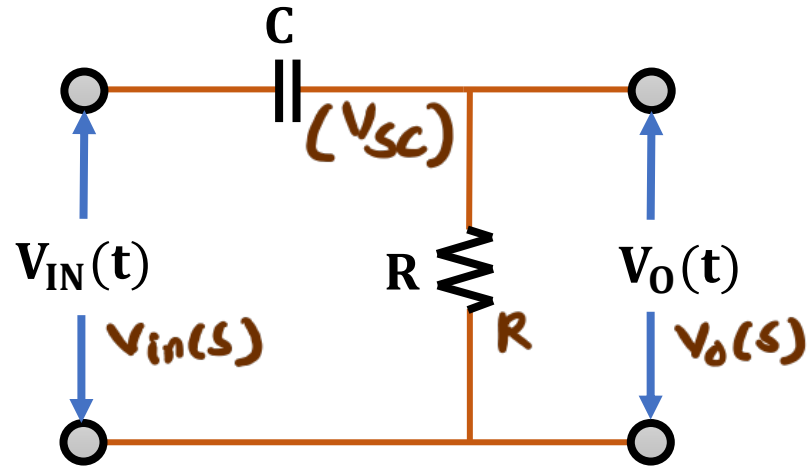Question 2 – Find the Transfer Function of a given (HPF) RC Circuit.



→ Zero initial cond.ⁿ


$$t = 0, V_C = 0$$

→ Transfer function $T(s) = \frac{V_o(s)}{V_{in}(s)}$

→ Apply voltage divider rule.


$$\Rightarrow V_o(s) = V_{in}(s) \left(\frac{R}{R + \frac{1}{sC}} \right)$$
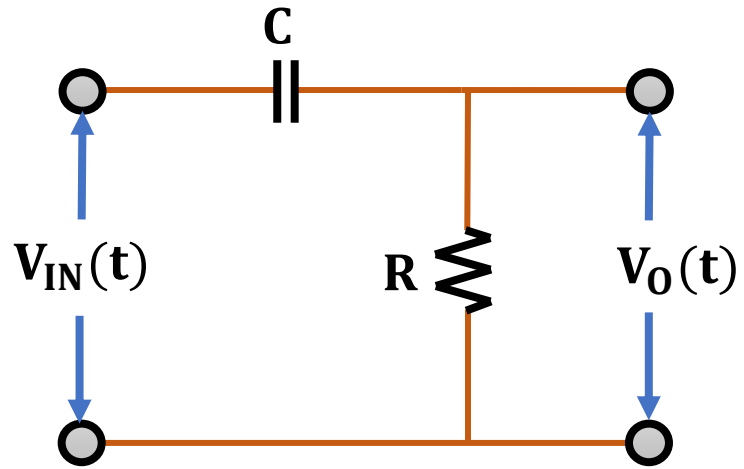
$$\Rightarrow \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{RSC}{1 + RSC}$$




$$\rightarrow X_C = \frac{1}{sC} = \frac{1}{j\omega C}$$

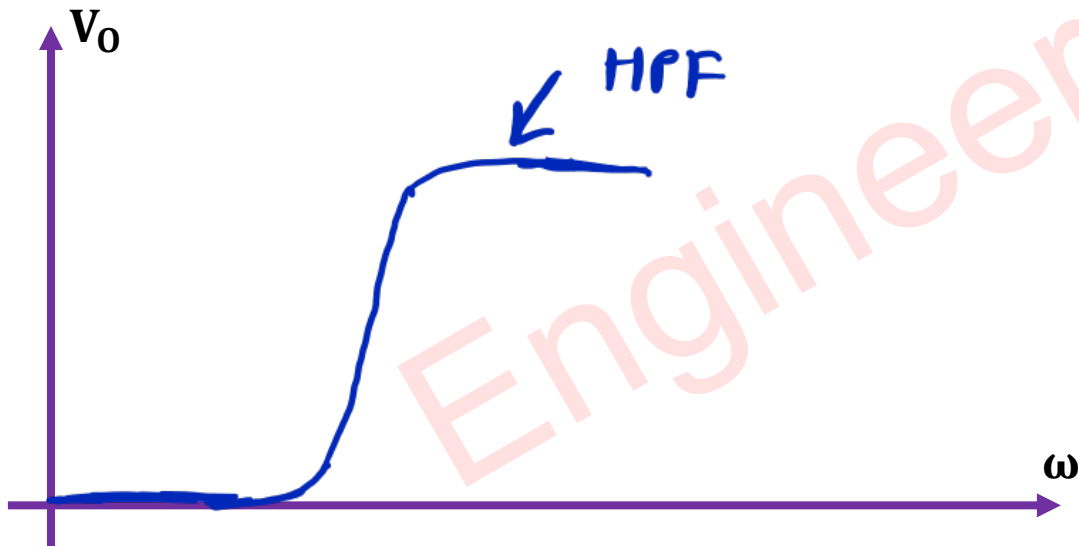$\rightarrow \omega \rightarrow 100, X_C = \text{high (O.C.)}, V_O \rightarrow 0$
 $\omega \rightarrow \text{high}, X_C = \text{low (S.C.)}, V_O \rightarrow V_{IN}$



Transfer Function of RL Circuits

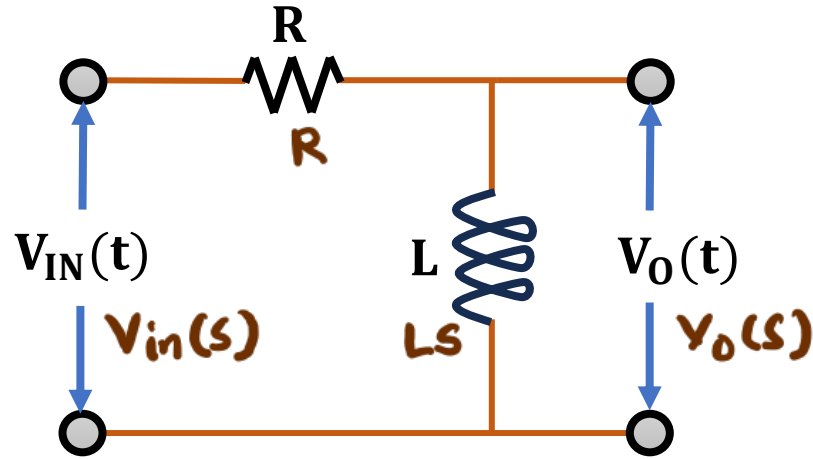Question 1 – Find the Transfer Function of a given (HPF) RL Circuit.



⇒ Zero initial cond.ⁿ


$$t=0, I_L = 0$$

⇒ Transfer function $T(s) = \frac{V_o(s)}{V_{in}(s)}$

⇒ Apply voltage divider rule.

$$\Rightarrow V_o(s) = V_{in}(s) \left(\frac{LS}{R + LS} \right)$$

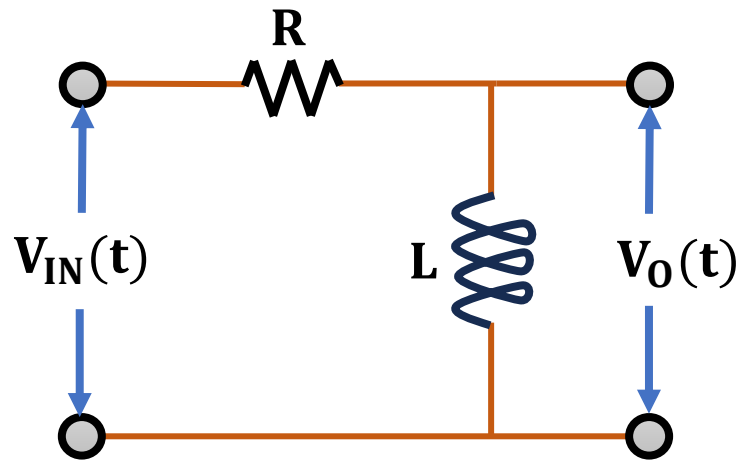
$$\Rightarrow \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{LS}{R + LS}$$




$$\leadsto X_L = \omega L = j\omega L$$

$\leadsto \omega \rightarrow \text{low}, X_L = \text{low (s.c.)}, V_O \rightarrow 0$

$\omega \rightarrow \text{high}, X_L = \text{high (o.c.)}, V_{in} \rightarrow V_O.$

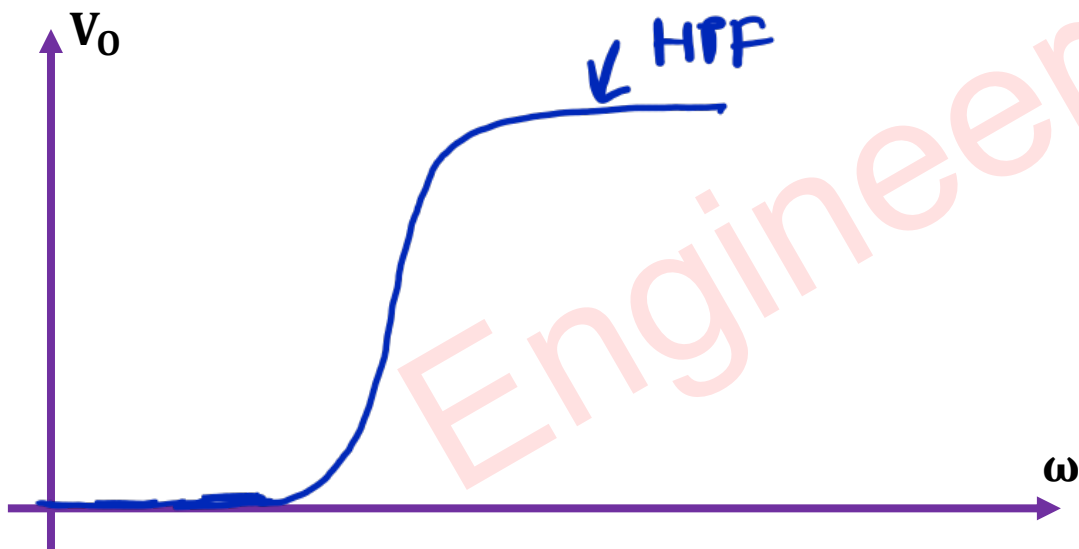

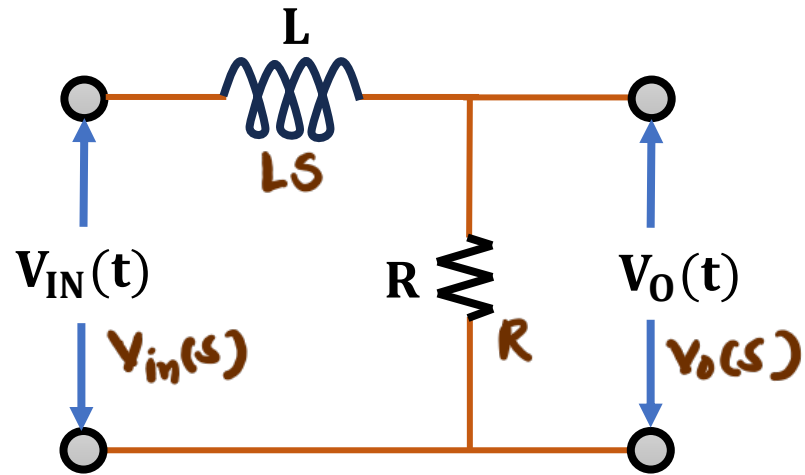Question 2 – Find the Transfer Function of a given (LPF) RL Circuit.



→ Zero initial cond.ⁿ


$$t = 0, I_L = 0$$

→ Transfer function $T(s) = \frac{V_o(s)}{V_{in}(s)}$

→ Apply Voltage divider rule.

$$\Rightarrow V_o(s) = V_{in}(s) \left(\frac{R}{R + LS} \right)$$

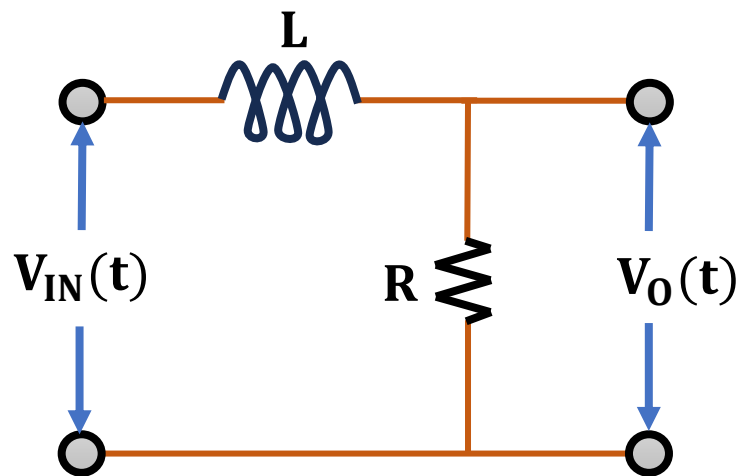
$$\Rightarrow \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{R}{R + LS}$$



$$\leadsto X_L = SL = j\omega L$$


$\leadsto \omega \rightarrow \text{low}, X_L = \text{low (s.c.)}, V_{in} \rightarrow V_o$

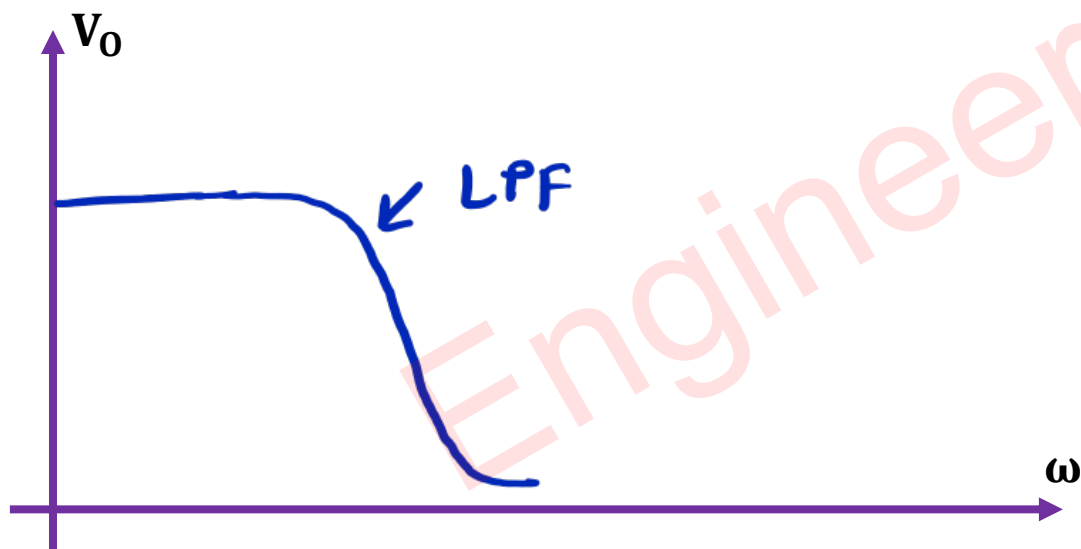$\omega \rightarrow \text{high}, X_L = \text{high (o.c.)}, V_o \rightarrow 0$



Transfer Function of RLC Circuits

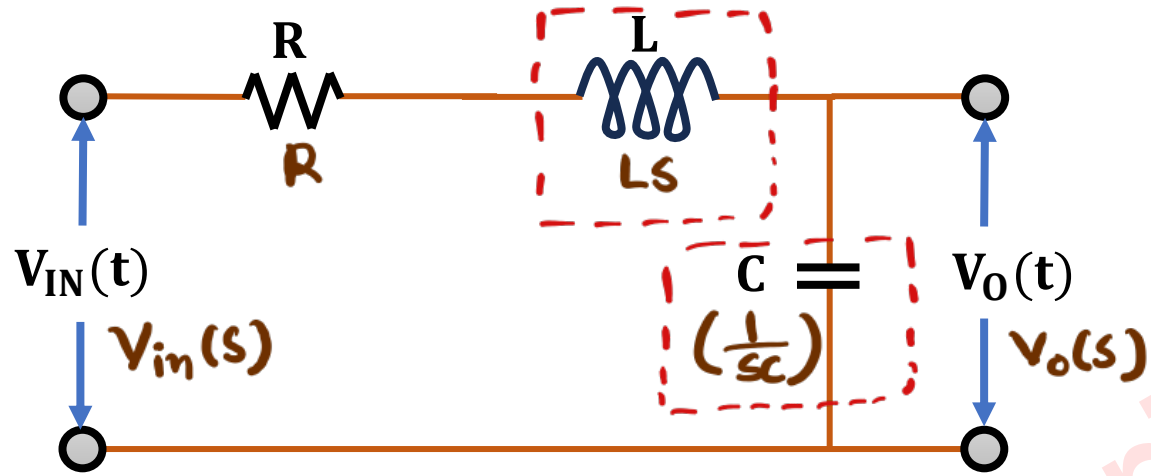Question 1 – Find the Transfer Function of a given RLC Circuit.



→ Apply zero initial cond.ⁿ

$$t=0, V_c = 0, I_L = 0$$

→ Transfer function

$$T(s) = \frac{V_o(s)}{V_{in}(s)}$$

→ Apply voltage divider rule.


$$\Rightarrow V_o(s) = V_{in}(s) \left[\frac{1/sC}{R + LS + 1/sC} \right]$$

$$\Rightarrow \frac{V_o(s)}{V_{in}(s)} = T(s) = \frac{1}{LCs^2 + RCs + 1}$$

↑
 s^2 means Order = 2

→ In circuit, we have two effective elements which can store energy. So order of system = 2

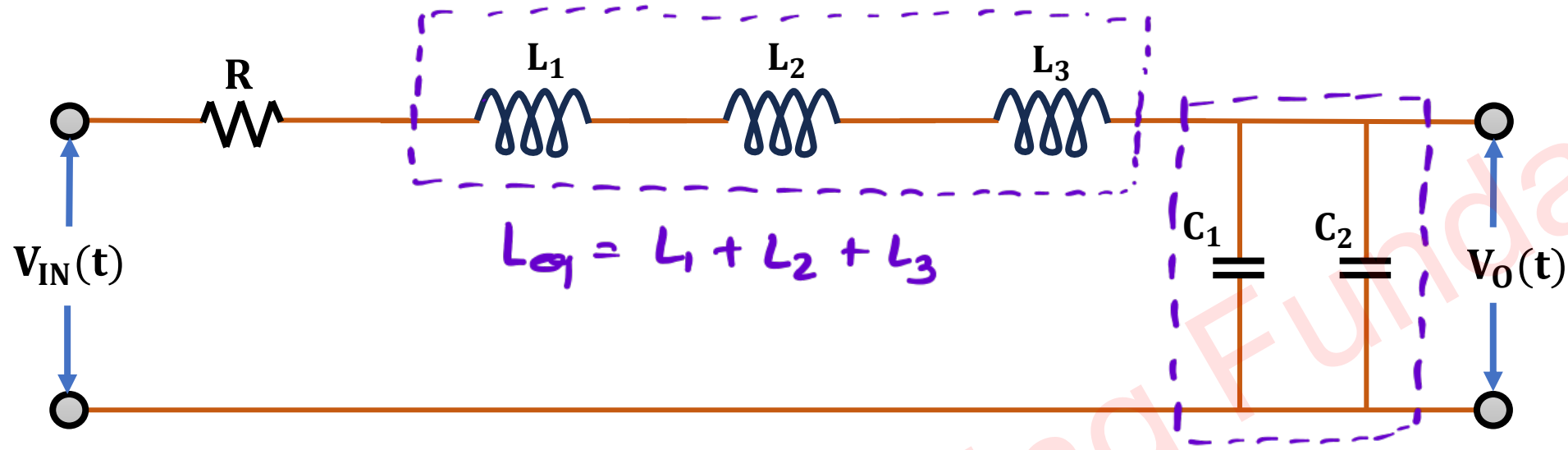Question 2 – Find the Order of the Circuit.




⇒ effectively, we have L_{eq} & C_{eq} .
So, order of the system is 2.

$$\Rightarrow T(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{L_{eq}C_{eq}s^2 + RC_{eq}s + 1}$$

$\uparrow$
 s^2 term

Transfer Function of Electrical N/W

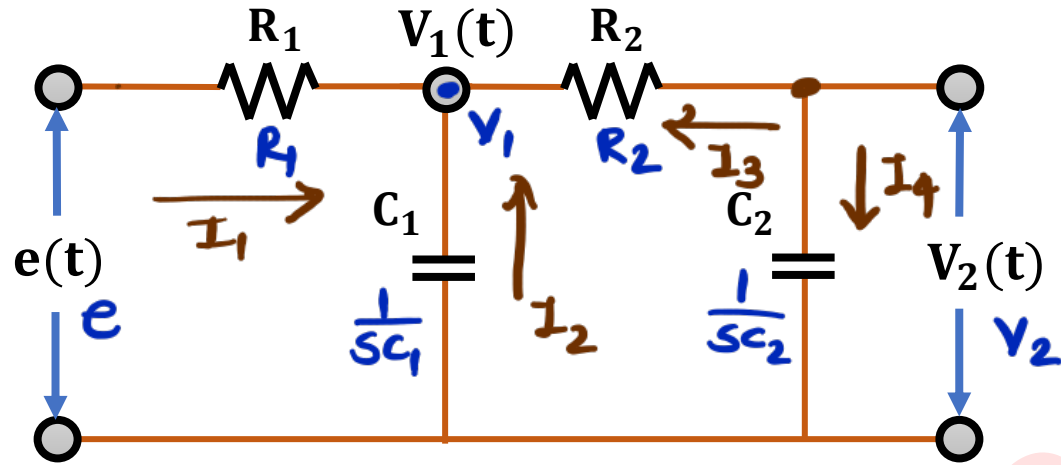Question – Find the Transfer Function of the Electrical Network. $\frac{V_2}{e} = ?$



~ Apply KCL at Node V_1

$$\Rightarrow I_1 + I_2 + I_3 = 0$$

$$\Rightarrow \frac{V_1 - e}{R_1} + \frac{V_1}{1/sC_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\Rightarrow V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} + sC_1 \right] = \frac{e}{R_1} + \frac{V_2}{R_2}$$

$$\Rightarrow V_1 [R_1 + R_2 + sC_1 R_1 R_2] = e R_2 + V_2 R_1$$

$$\Rightarrow V_1 = \frac{e R_2 + V_2 R_1}{R_1 + R_2 + sC_1 R_1 R_2} \quad \text{--- (1)}$$

~ Apply KCL at Node V_2

$$\Rightarrow I_3 + I_4 = 0$$

$$\Rightarrow \frac{V_1 - V_2}{R_2} + \frac{-V_2}{1/sC_2} = 0$$

$$\Rightarrow \frac{V_1}{R_2} = V_2 \left[\frac{1}{R_2} + sC_2 \right]$$

$$\Rightarrow V_1 = V_2 [1 + SC_2 R_2] \text{ --- (2)}$$

$\Rightarrow$ Put (1) into (2)

$$\Rightarrow \frac{e R_2 + V_2 R_1}{R_1 + R_2 + SC_1 R_1 R_2} \times \frac{1}{1 + SC_2 R_2} = V_2$$

$$\Rightarrow \frac{e R_2}{(1 + SC_2 R_2)(R_1 + R_2 + SC_1 R_1 R_2)} = V_2 \left[1 - \frac{R_1}{(1 + SC_2 R_2)(R_1 + R_2 + SC_1 R_1 R_2)} \right]$$

$$\Rightarrow e R_2 = V_2 [(1 + SC_2 R_2)(R_1 + R_2 + SC_1 R_1 R_2) - R_1]$$

$$\Rightarrow \boxed{\frac{V_2}{e} = \frac{R_2}{(1 + SC_2 R_2)(R_1 + R_2 + SC_1 R_1 R_2) - R_1}}$$